


CE/CZ1005 Digital Logic

Tutorial 8


 
- Q1. Using a behavioural description, write a Verilog module that has three 8-bit inputs, *a*, *b*, and *c*, and outputs the largest (max) and smallest (min) of them. Add a third output (*diff*) that outputs the difference between the two. You should use if statement(s). You can ignore equal inputs.
- Q2. The *clk* input in the timing diagram is connected to the control/enable/clk input of the following circuits:
- SR-latch (no enable/control)
 - Enabled SR-latch
 - Enabled D-type latch
 - JK flip-flop
 - D flip-flop

For the D-type latch and D flip-flop, the *in1* input is connected to the D input, and *in2* is left disconnected. For the SR-latches, *in1* is connected to the S input and *in2* is connected to the R input. For the JK flip-flop, *in1* is connected to the J input and *in2* is connected to the K input.

Complete the timing diagram showing the outputs of the four sequential circuits. Indicate any undefined output by shading the relevant area.



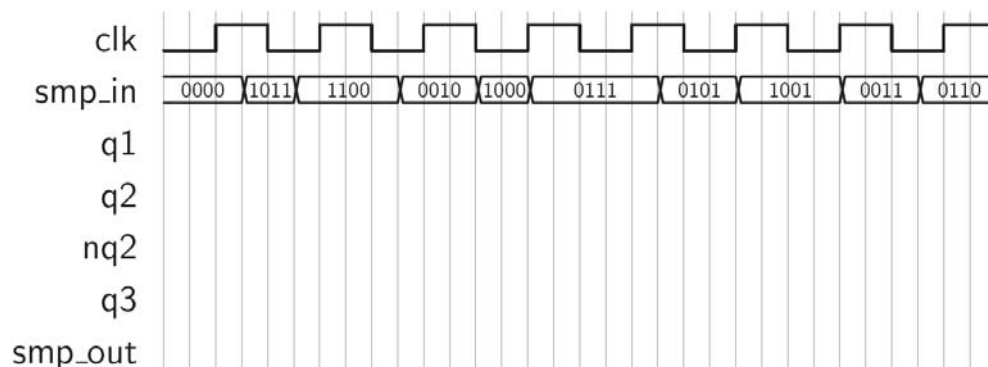 - Q3. A bank of 4-bit registers is arranged as per the diagram below, to form a FIFO, with a bitwise inversion in the middle. The input shown in the diagram is applied to the leftmost register. All registers share the same clock. Show a timing diagram for the output at the rightmost register. A bitwise inversion simply inverts each bit of the signal individually. Write down the resulting hexadecimal number sequence at the output.



Q1.

```
module compmod (input [7:0] a, b, c,  
                output reg [7:0] max, min,  
                output [7:0] diff);  
  
    assign diff = max - min;  
  
    always @ * begin  
        if (a>b) begin  
            if (c>a) begin  
                min = b;  
                max = c;  
            end  
            else begin  
                max = a;  
                if (c>b) min = b;  
                else min = c;  
            end  
        end  
        else begin  
            if (c>b) begin  
                min = a;  
                max = c;  
            end  
            else begin  
                max = b;  
                if (c>a) min = a;  
                else min = c;  
            end  
        end  
    end  
endmodule
```

Note: it is very easy to make syntax errors when using nested conditional if statements.

Q2

The rules:



SR-Latch: ignore clk, when S (in1) is high, set to 1, when R (in2) is high, set to 0, when both are high, undefined output, that may go metastable on de-assertion.

Enabled SR-latch: As above, but only consider inputs when clk is high

Enabled D-latch: When clk is high, in1 should pass to the output


JK-flip-flop: output only changes at edges of clk. J (in1)=1 sets output high, K(in2)=1 sets output low, Both J and K 1 toggles output. But all only considered at clock rising **edge**.

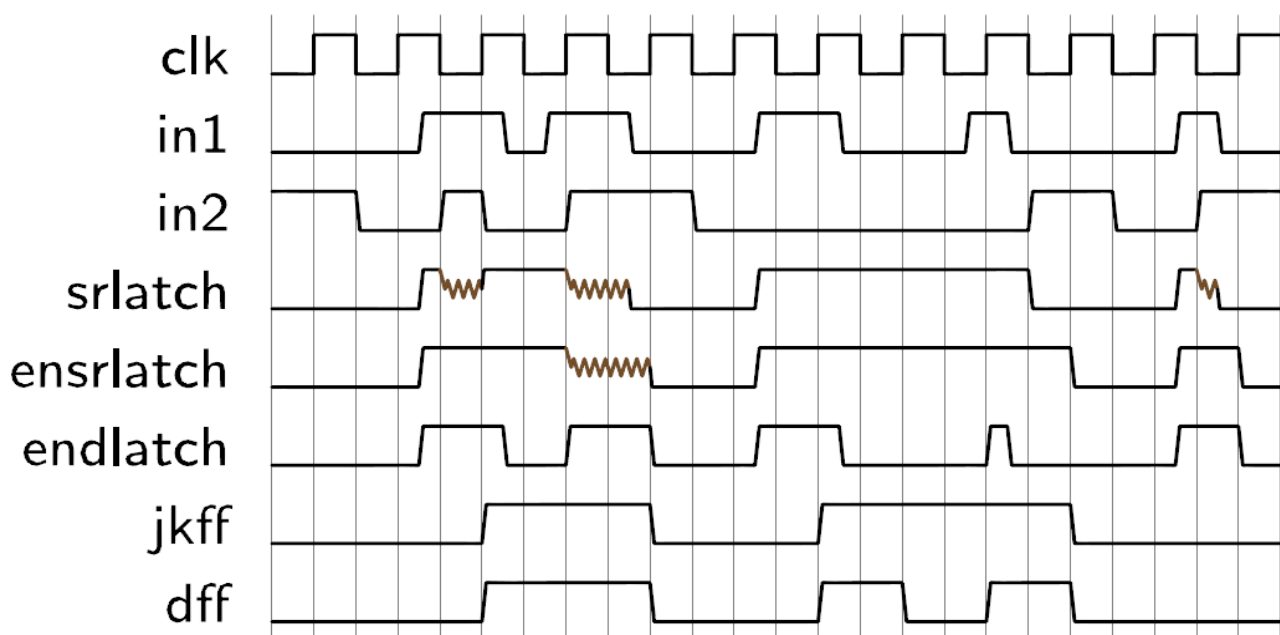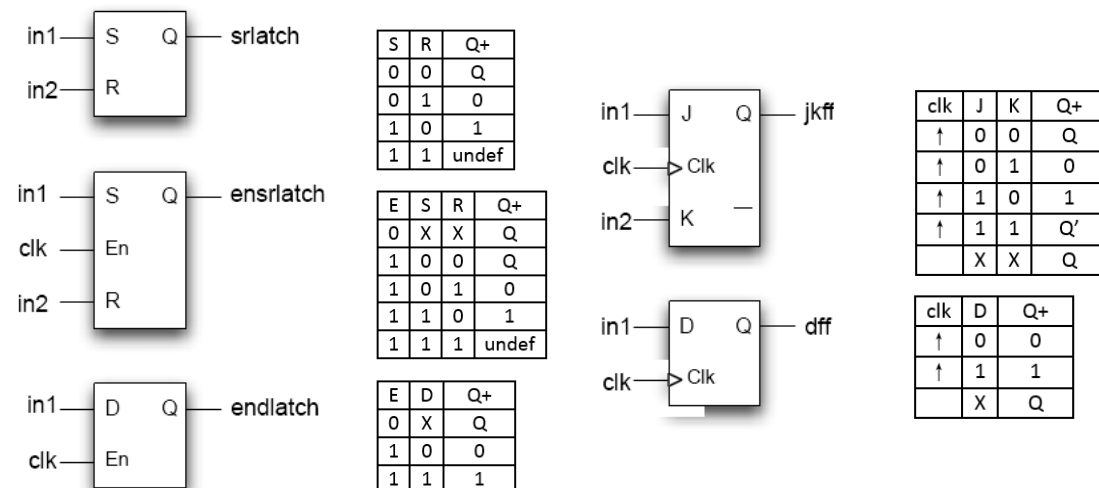D-flip-flop: at rising edge, output will change to follow D (in1) input at that instance.



Note: the output of an SR latch is undefined if the S and R inputs are both 1.

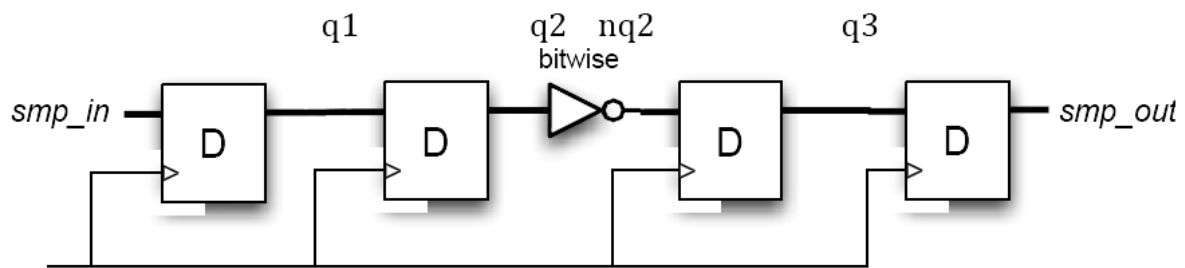Q3. The extra signals in the timing diagram should give a hint to how to do this, i.e. one step at a time. Annotate the diagram:



Remember each register's output only changes at the rising edge. Hence, some inputs are missed. Important to remember that the input value passed to the output is the one **just** before the rising edge.

