


# **CX1005**

## **Digital Logic**

### Verilog Recap
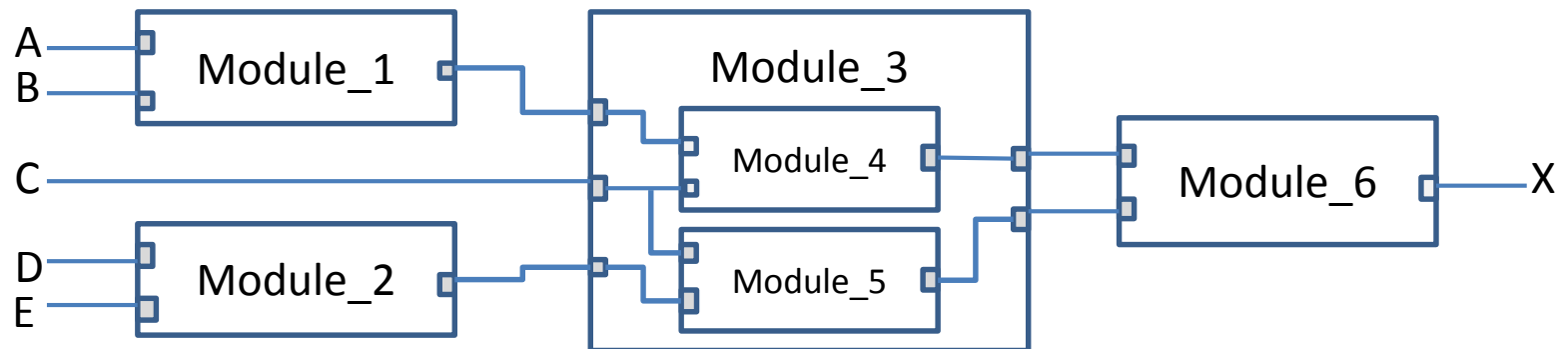
# Verilog Hardware Description Language


- Language with special constructs for describing hardware
- The most important rule when thinking about Verilog design, is to think *in hardware*
- In Verilog, designs are broken down into **modules**
- Modules can contain code to describe hardware and also instances of other modules


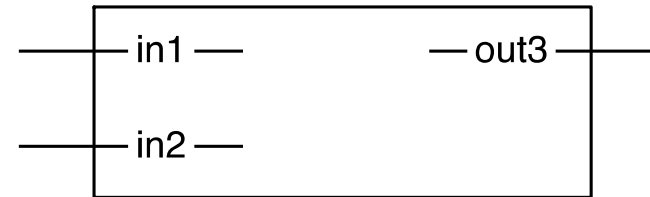
## Ports, Wires, Reg


- Ports act exactly like wires:
  - Can “read” the value of an input or output port
  - But can only “assign”/“write” to an output port

```
module simple (input in1, in2,  
               output out3);  
endmodule
```



- Regs are exactly the same as wires, but **can only be assigned to from within always blocks**
  - Can be “read” anywhere

 
```
module simple (input [3:0] in1,  
               input in2,  
               output out3);  
    wire thing;  
    wire [3:0] what;  
    reg that;  
    reg [1:0] there;  
endmodule
```


 
## Ports, Wires, Regs

- Internal wires are just anchor points to which you can connect logic:
- What will this do?


```
module nothing (input a_in,  
                output a_out);  
  
    wire w1, w2, w3, w4, w5;  
  
    assign w1 = a_in;  
    assign w2 = w1;  
    assign w3 = w2;  
    assign w4 = w3;  
    assign w5 = w4;  
    assign a_out = w5;  
  
endmodule
```


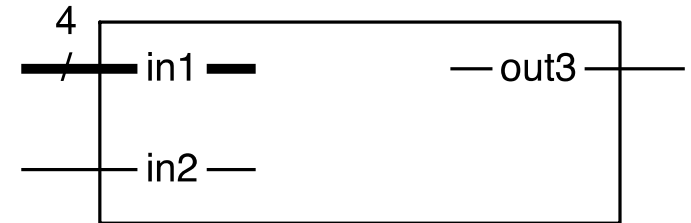
## Ports, Wires, Regs


- Any port, wire, or reg can be declared multi-bit by preceding its name with an index range:

```
module simple (input [3:0] in1,
               input in2,
               output out3);
endmodule
```



- We can slice sections or single bits of any port, wire, or reg and use them as we do for single wires:

 
```
module simple (input [3:0] in1,
               output out3);
    assign out3 = in1[2];
endmodule
```


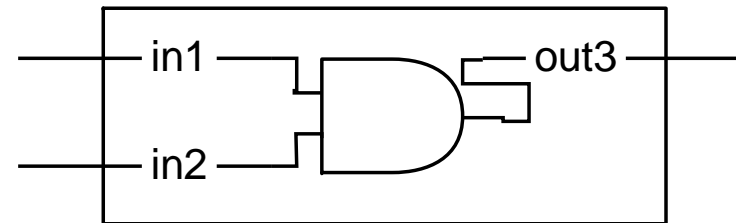
## Instantiating Gate-Level Primitives


- We can connect ports/wires/reg by instantiating primitives or modules:

```
module simple (input in1, in2,  
               output out3);  
  
    and a1 (out3, in1, in2);  
  
endmodule
```





- You never want to assign, by any means, to a wire, port, or reg multiple times:
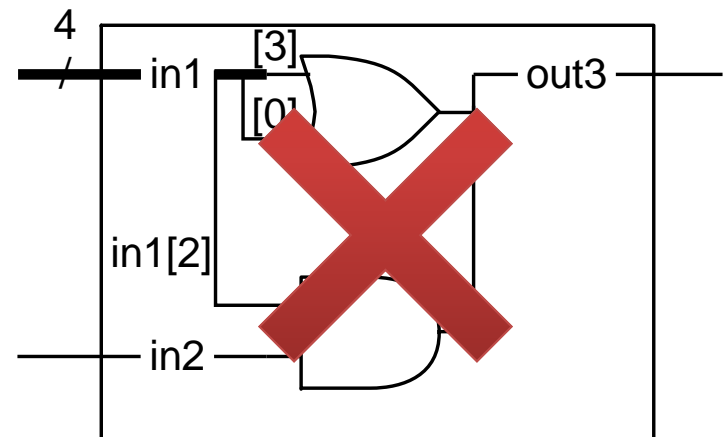
```
module simple (input [3:0] in1,  
               input in2,  
               output out3);  
  
    and (out3, in1[2], in2);  
    or  (out3, in1[3], in1[0]);  
endmodule
```


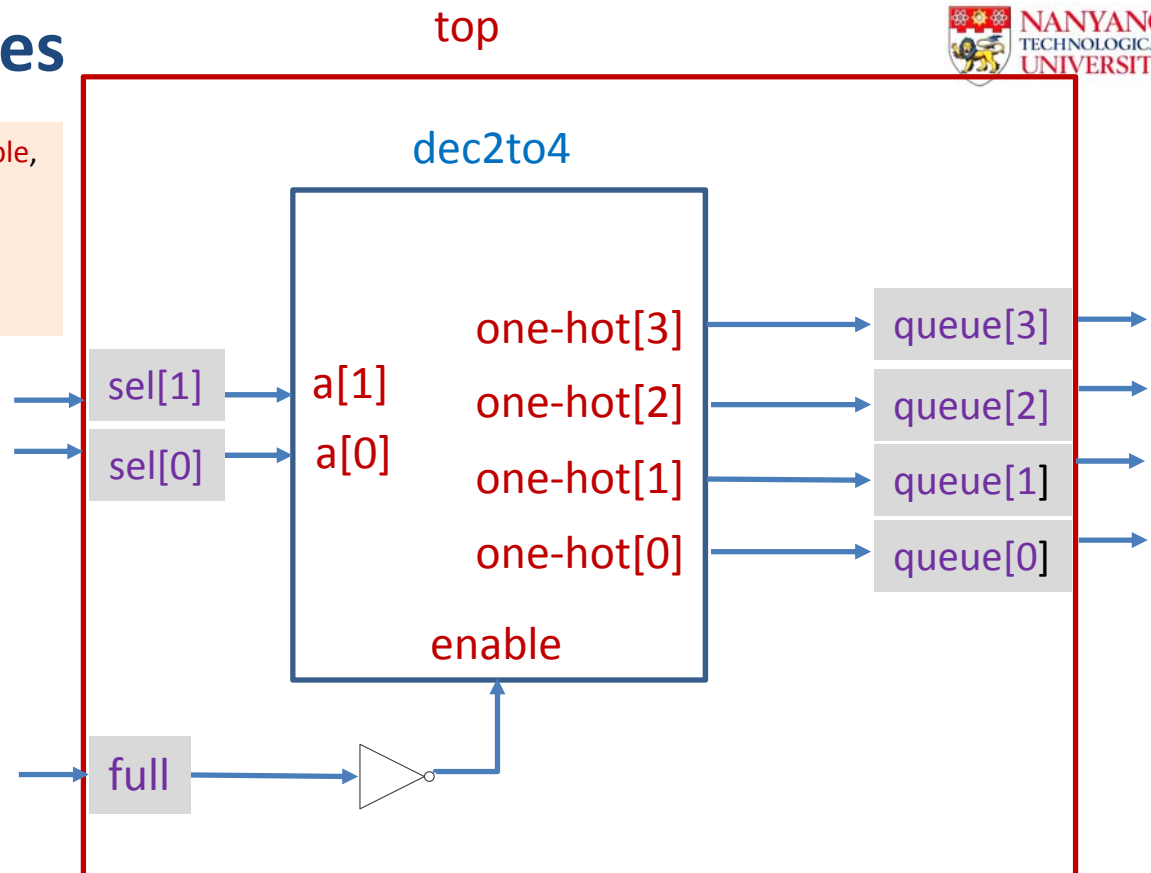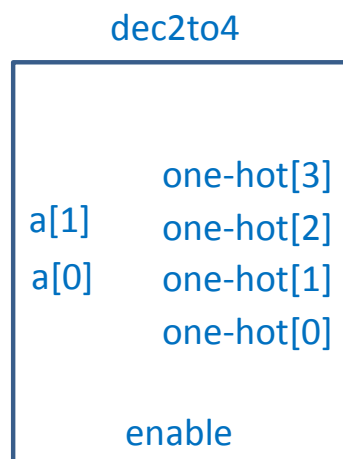
# Instantiating Modules

```
module dec2to4 (input [1:0] a, input enable,
               output [3:0] one-hot);
...
endmodule
```



```
module top (input [1:0] sel,
            input      full,
            output [3:0] queue);


    dec2to4 (.a(sel), .enable(~full), .one-hot(queue));

endmodule
```
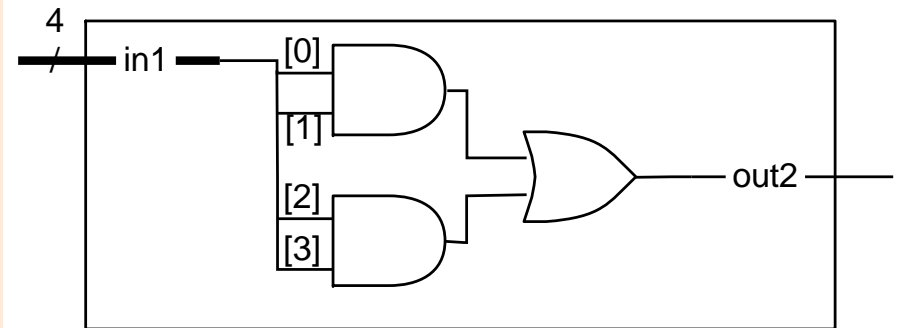
# Assign Statements

- These are the same:

```
module simple (input [3:0] in1,  
               output out2);  
  
    and (w1, in1[0], in1[1]);  
    and (w2, in1[2], in1[3]);  
    or  (out2, w1, w2);  
  
endmodule
```



```
module simple (input [3:0] in1,  
               output out2);  
  
    assign out2 = ((in1[0] && in1[1]) ||  
                  (in1[2] && in1[3]));  
  
endmodule
```




## Assign Statements

- Assign statements let us assign the result of an expression to a signal
- Allow us to use many more operators
  - Bitwise or Logical
  - Comparisons and equality
  - Arithmetic
- This is always preferred to instantiating gates or simple low-level modules
- Remember, you cannot assign to regs!
  - Reg can only be assigned within an always block

```
reg temp;
```

```
assign temp = 1'b0;
```

 

~	(bitwise NOT)
&	(bitwise AND)
	(bitwise OR)
^	(bitwise XOR)
~^ or ^~	(bitwise XNOR)

!	(logical NOT)
&&	(logical AND)
	(logical OR)


<	(less than)
<=	(less than or equal to)
>	(greater than)
>=	(greater than or equal to)
==	(equal to)
!=	(not equal to)

+	(addition)
-	(subtraction)
*	(multiplication)
/	(division)
%	(modulus)

## Conditional Assignment


- One other trick with the assign statement is conditional assignment
- Creates a multiplexer, like an if/else statement:

```
assign y = x ? a : b;
```

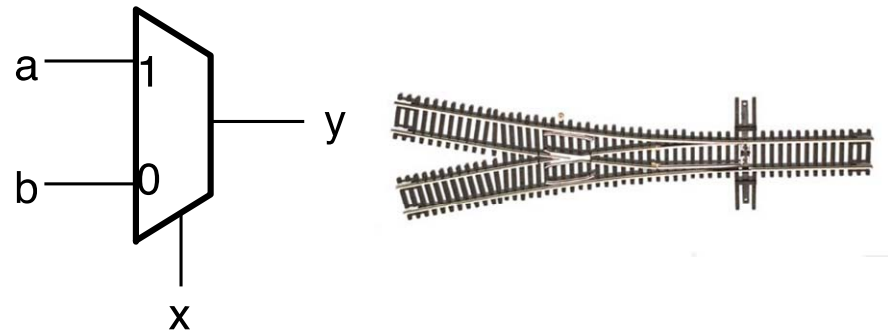

- Any expression in the body of the conditional assignment is also generated as hardware


```
assign y = x ? a & b : b & c;
```

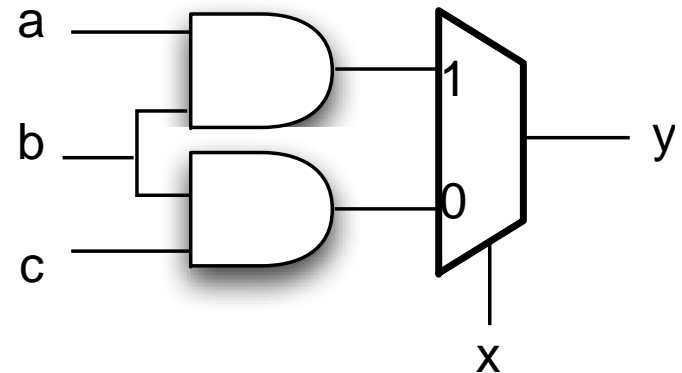
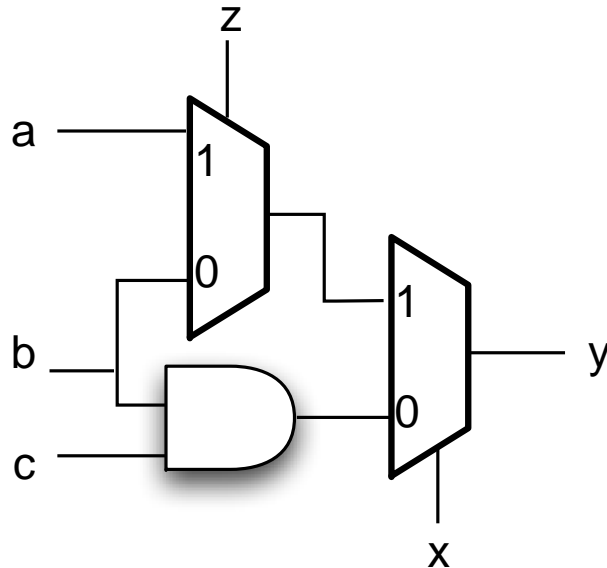
## Conditional Assignment


- Those expressions can themselves be conditional assignments (Brackets make this easier to read)

```
assign y = x ? (z ? a : b) :  
              b & c;
```



- Everything in an assign statement gets turned into a mini combinational circuit
  - The signal being assigned to is the output of this mini circuit
  - The tools take care of how best to design the circuit
- Conditional assignment simply adds a multiplexer to select which expression to finally route to the assigned signal


# Overview of Structural Design

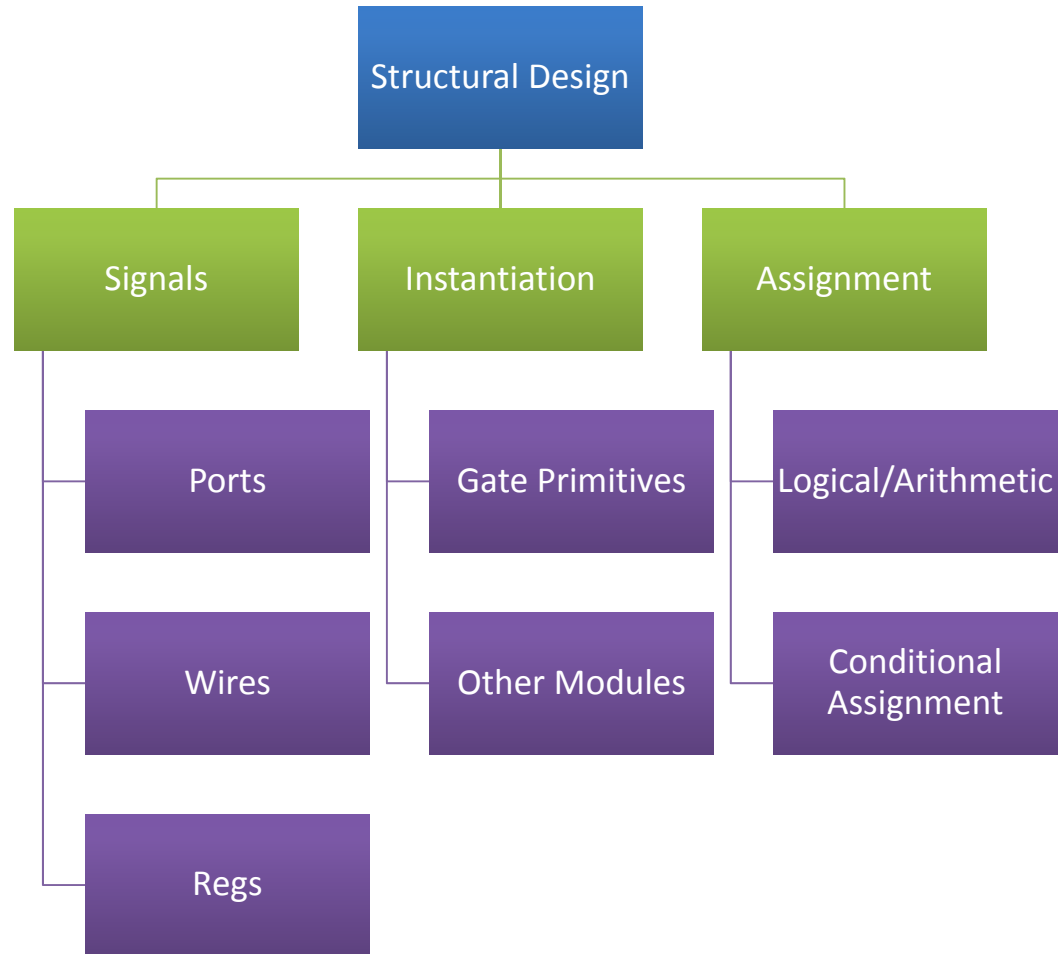
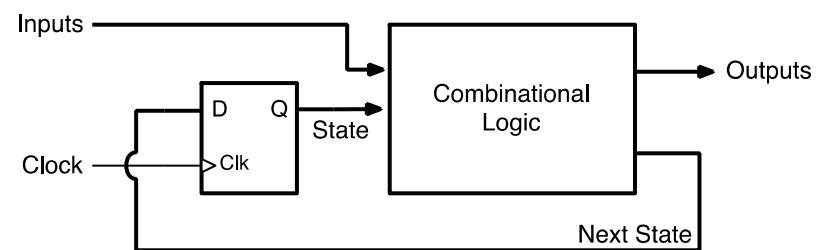
## Behavioral Design

- In behavioral design, we raise the level of our description and rely on the synthesis tools to do more
- We use the **always** block to describe circuits behaviorally
- We can design both **combinational** and **sequential** circuits using always blocks
- Always block is effectively a super-mega assign statement
- There is no other way to build synchronous blocks

```
always @ *  
begin  
    a = ... ;  
    b = ... ;  
end  
  
assign c = ... ;  
  
always @ (posedge clk)  
begin  
    y <= ... ;  
    x <= ... ;  
end  
  
assign z = ... ;
```



## Combinational Always Blocks

- Has a list of signals in its sensitivity list, or better: \*
- Can assign to one or more signals
- Must only assign to reg signals
- We use a blocking assignment (=)
- **Statement order** within the always block does **matter**
- Each assignment results in a combinational circuit
- If and case statements are very useful
- All signals to which it assigns must be assigned in all possible cases

```
module gate2 (input a, b, c,  
              output reg y);
```

```
    reg x;
```


```
    always @*
```

```
    begin
```

```
        x = a & b;
```

```
        y = x ^ c;
```

```
    end
```

 

```
endmodule
```

```
module mux4 (output reg q,  
             input [3:0] d,  
             input [1:0] sel);
```

```
    always @* begin
```

```
        case (sel)
```

```
            2'b00 : q = d[0];
```

```
            2'b01 : q = d[1];
```

```
            2'b10 : q = d[2];
```

```
            2'b11 : q = d[3];
```


```
        endcase
```

```
    end
```

```
endmodule
```

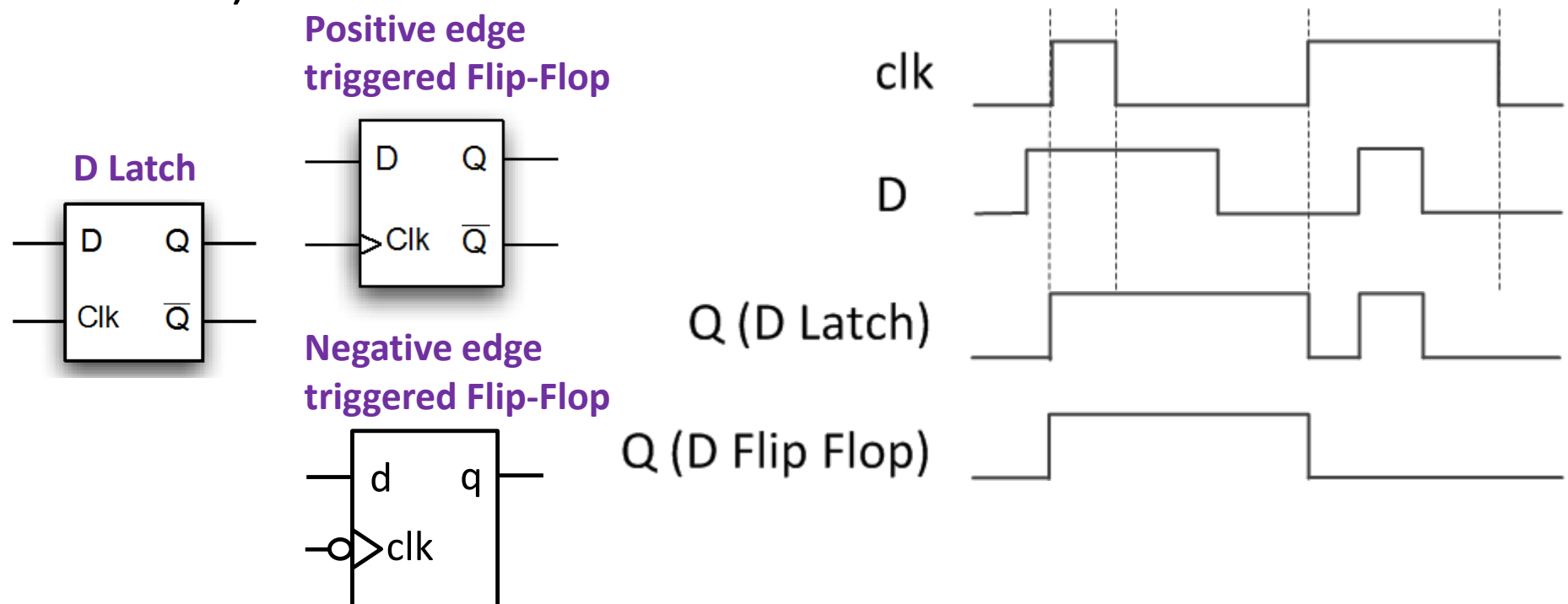
# Sequential Circuits

- Sequential circuits are any circuits that have the concept of state: include latches, flip-flops, etc.
- Latches are **level-sensitive**, i.e., their outputs change when the control (enable) input is high
- A flip-flop/register is **edge-sensitive**, i.e. their outputs change at the rising/falling edge of the control (enable)
- Modern design is almost always synchronous (one shared clock)


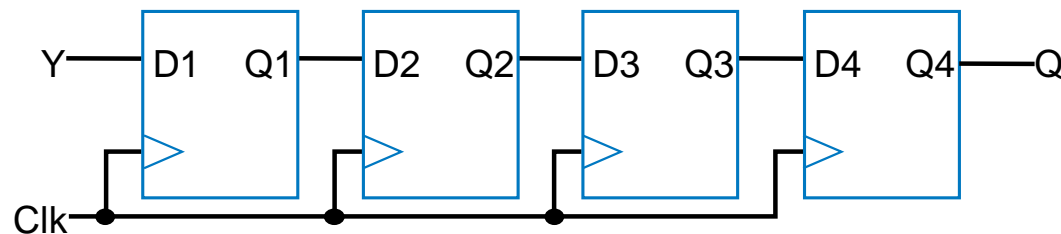
## Synchronous Always Block

- Use ***posedge*** *clk* in its sensitivity list
- Can assign to one or more signals
- Must only assign to reg signals
- Each assigned signal becomes a register connected to any logic given in the expressions
- We use non-blocking assignment (***<=***)
- **Statement order does not matter** with non-blocking assignments
- We should ensure all registers respond to a reset




```
reg q1, q2, q3, q;  
  
always@(posedge clk)  
begin  
    if (rst) begin  
        q1 <= 1'b0;  
        q2 <= 1'b0;  
        q3 <= 1'b0;  
        q  <= 1'b0;  
    end  
    else begin  
        q1 <= y;  
        q2 <= q1;  
        q3 <= q2;  
        q  <= q3;  
    end  
end
```



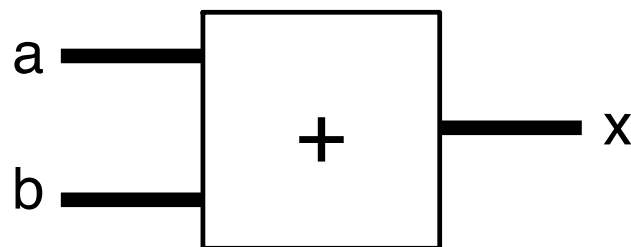
# Combinational and Synchronous

- Identical statements produce the same circuit, but with a synchronous always, we get a register on the end:

```
always @ *
begin
    x = a + b;
end
```


 
```
always @ (posedge clk)
begin
    if (rst)
        x <= 6'b000000;
    else
        x <= a + b;
end
```



# Combinational and Synchronous

```
always @ *
```

```
begin
```

```
    x = a + b;
```

```
    y = x * x;
```

```
end
```



```
always@(posedge clk)
```

```
begin
```


```
    z <= x;
```

```
    r <= z * z;
```

```
end
```

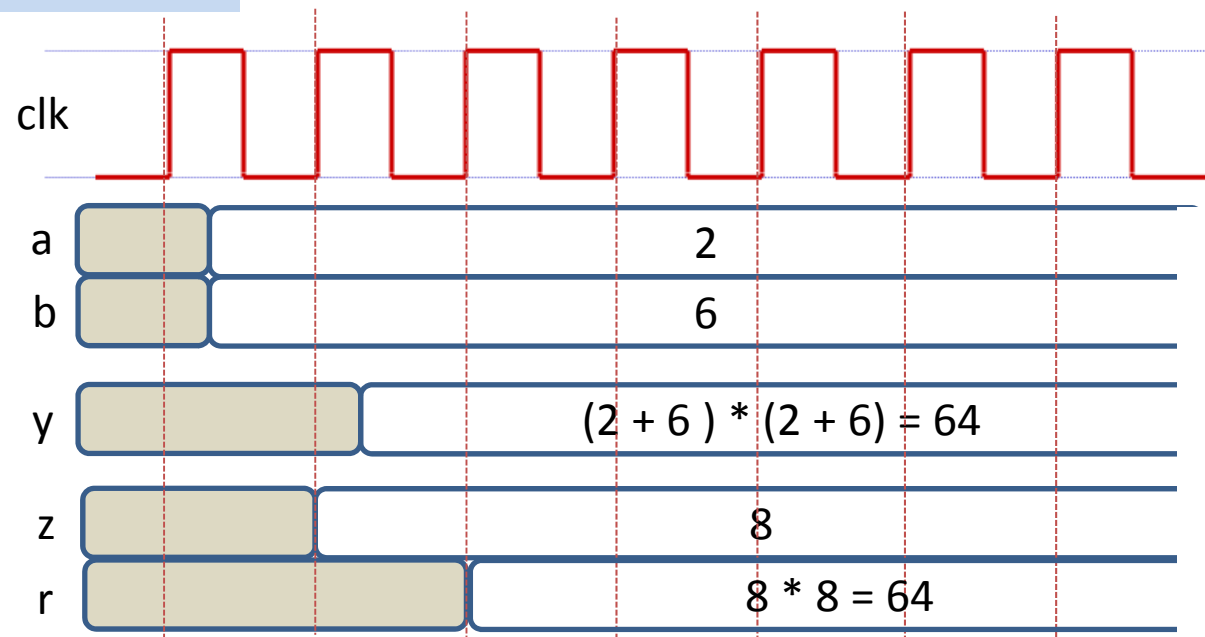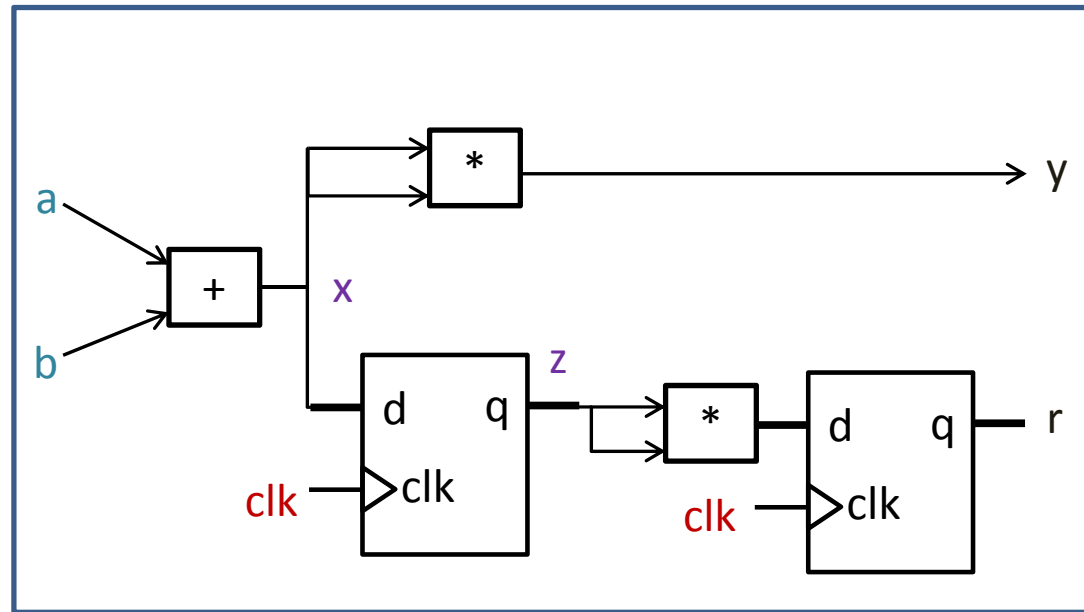


# Behavioral Verilog

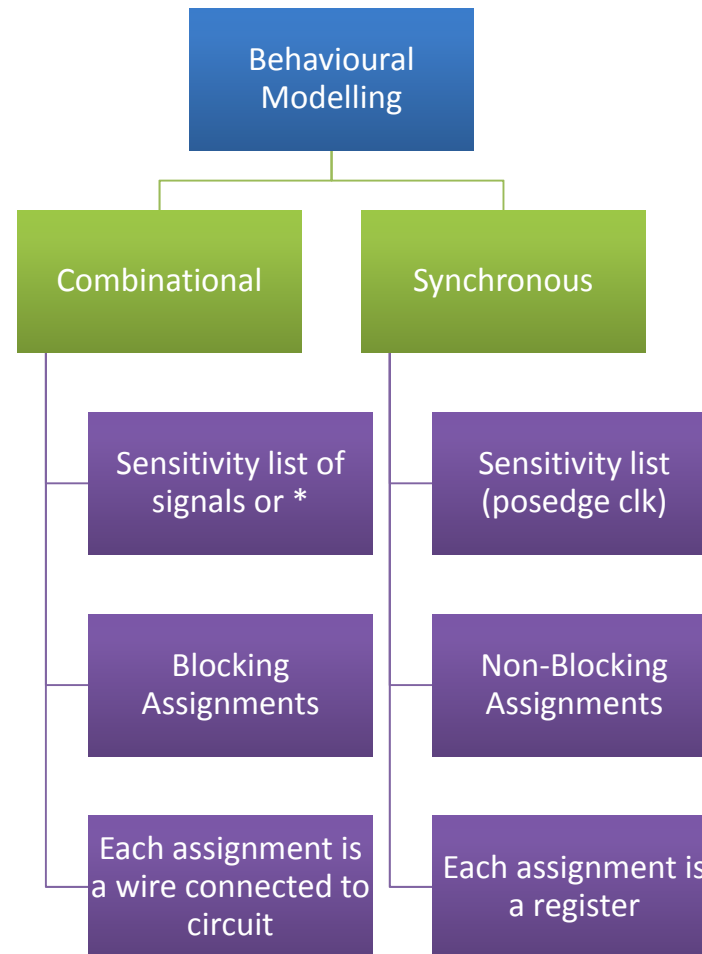
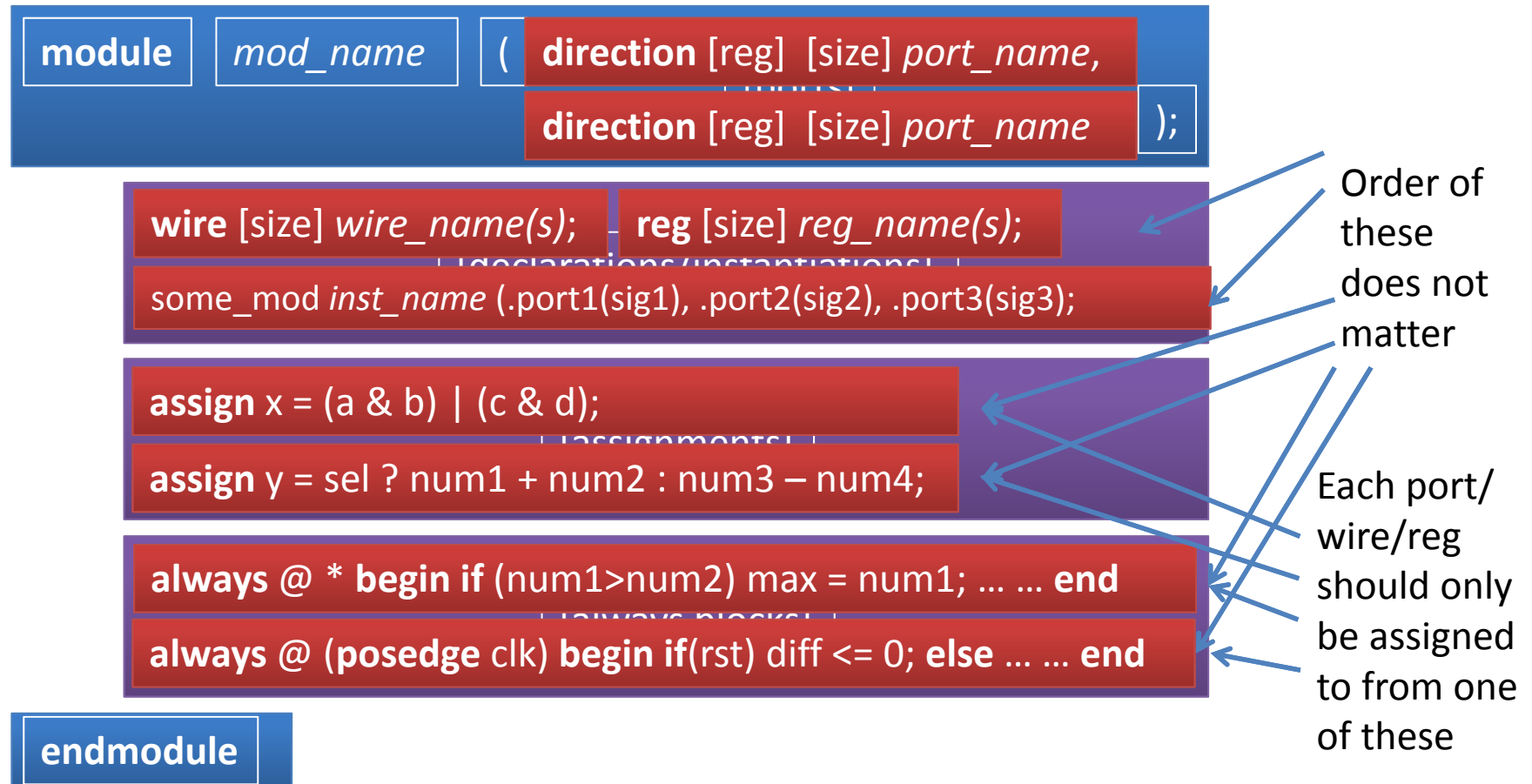
# Code structure

- This general structure for a module should help:



# Verilog Summary

- Think in terms of hardware blocks, not instructions
- Think of block descriptions, not programs
- If you can't understand what the circuit will look like, likely it won't work
- There are many ways to achieve the same thing
  - Go for simplicity
  - Split things up when they get unwieldy
- We have not covered everything:
  - Simulation and verification
  - Non-synthesizable constructs