

# **E-learning week self-study materials**


**Please go through these materials on your own during the e-learning/recess week**

**You may post questions on the edventure discussion board or email Dr Chan if you have questions regarding these contents**

- **IEEE logic symbols**
- **CMOS transmission gate**
- **CMOS 2-input multiplexer**


# IEEE/ANSI Standard Logic Symbols

- use rectangular symbols
- bubbles replaced by small triangles or wedges (**think 0**)
- Students are required to recognise these symbols but not required to draw these symbols

 


**Fig. 3-41: Traditional and IEEE logic symbols  
(Tocci 10<sup>th</sup> ed)**

  
Output is 0 when “the single input” is 1




Output is 1 when “the single input” is 1




Output is 1 when “all the inputs” are 1

 


Output is 0 when “all the inputs” are 1

 

 
**Output is 1 when “at least one input is” 1**



 
**Output is 0 when “at least one input” is 1**



 Output is 1 when “exactly one input” is 1



 Output is 0 when “exactly one input” is 1



# IEEE/ANSI Standard Logic Symbols


## How to interpret

- The symbol inside the rectangle specifies the requirement on the inputs
- **&** : “all the inputs”
- **1** : “the single input” – only true for a buffer or an inverter
- **$\geq 1$**  : “at least one input”
- **=1** : “exactly one input” – e.g. on a 2-input XOR gate


 
## Example 1: CMOS transmission gate

- Section 3.7.1 of textbook by Wakerly
- 1 PMOS and 1 NMOS transistors can be connected in parallel to form a logic-controlled switch.
- When  $S=0$  ( $S'=1$ ), both transistors are off. Output  $f$  is effectively disconnected from input  $X$ .  $f$  is at **high impedance**.
- When  $S=1$  ( $S'=0$ ), both transistors are on. Output  $f$  is effectively connected to input  $X$ .




(a) Circuit


$s$	$f$
0	Z
1	$x$

(b) Truth table

**Z means  
High  
impedance**

 


(c) Equivalent circuit

 


(d) Graphical symbol

**Fig. 3-45: CMOS transmission gate**
 
## Example 2: Two-input multiplexer using CMOS transmission gates




**Logic symbol**

 


## Circuit analysis: when $S=0$

- When  $S=0$

 


# Circuit analysis: when $S=0$ , only upper transmission gate conducts.

- When  $S=0$ ,
- Output  $Z=X$

 


## Circuit analysis: when $S=1$

- When  $S=1$

 


# Circuit analysis: when $S=1$ , only lower transmission gate conducts.

- When  $S=1$ ,
- Output  $Z=Y$

 
 
# Two-input multiplexer using CMOS transmission gates: truth table



**Logic symbol**

Input S	Ouput Z
0	X
1	Y

**Truth Table**